



Model Answer

Attempt all questions, full mark: 100 Points

Time: 3 Hours

Question #1: (12 Points)

The circuit shown in Fig.1 is used to measure the change in resistance experienced by strain gages.

- Derive an expression for the output voltage V_{out} in terms of the resistance values and the reference voltage V_{ref} , assuming ideal op-amp and neglecting ΔR^2 w.r.t. R^2 . (8 Points)
- If $R = 160 \Omega$, $\Delta R = 1 \Omega$, $R_f = 1.2 \text{ K}\Omega$, and $V_{ref} = 8 \text{ V}$; find the value V_{out} . (4 Points)

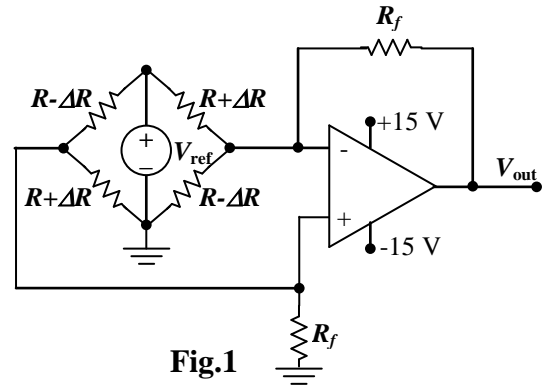


Fig.1

Expression for V_{out} :

$$V_{out} = \frac{2R_f \Delta R}{R^2} \cdot V_{ref}$$

Value of V_{out} :

$$V_{out} = 0.75 \text{ V}$$

Question #2: (16 Points)

In the circuit shown in Fig.2, the initial currents in inductors L_1 and L_2 are 8A and 1A respectively. The switch is opened at $t = 0$.

- Find $i(t)$, for $t \geq 0$. (8 Points)
- Find $v(t)$, for $t \geq 0$. (2 Points)
- Find $i_1(t)$ and $i_2(t)$, for $t \geq 0$. (4 Points)
- Determine the total energy stored in the inductors as $t \rightarrow \infty$. (2 Points)

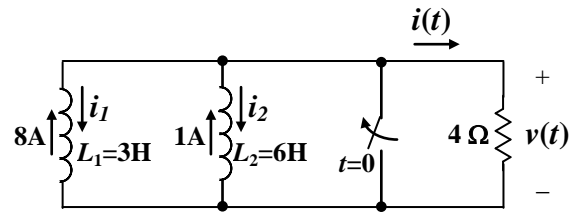


Fig.2

$$i(0^+) = 9 \text{ A}$$

$$i(\infty) = 0$$

$$\tau = 0.5 \text{ S}$$

$$i(t) = 9 e^{-2t} \text{ A}$$

$$v(t) = 36 e^{-2t} \text{ V}$$

$$i_1(t) = -2 - 6 e^{-2t} \text{ A}$$

$$i_2(t) = 2 - 3 e^{-2t} \text{ A}$$

$$\text{Energy stored in the inductors as } t \rightarrow \infty = 18 \text{ J}$$

Question #3: (12 Points)

The switch in the circuit shown in Fig.3 has been in position (a) for a long time. At $t = 0$, it moves to position (b). Find $i(0^+)$, $v_c(0^+)$, $di(0^+)/dt$, the roots of the characteristic equation s_1, s_2 and $i(t)$ for $t \geq 0$.

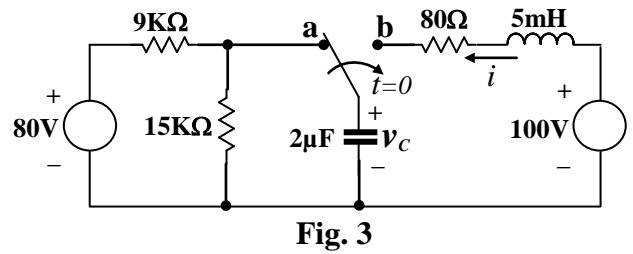


Fig. 3

$i(0^+) = 0$

$v_c(0^+) = 50 \text{ V}$

$di(0^+)/dt = 10^4 \text{ A/S}$

$s_1 = -8000 + j 6000$

$s_2 = -8000 - j 6000$

$i(t) = 1.6736 e^{-8000t} \sin(6000t) \text{ A}$

Question #4: (12 Points)

A three-phase Δ -connected -ve sequence source having the phase voltage $V_{ab}=240\angle 0^\circ \text{V}$ and negligible source resistance. The source supplies a resistive unbalanced Δ -connected load having impedances: $R_{AB}= 60 \Omega$, $R_{BC}= 40 \Omega$, and $R_{CA}= 80 \Omega$. The three lines connecting the source to the load have negligible resistances. The load power is measured using the two wattmeter method. The first wattmeter W_1 is connected between lines A and B, while the second one W_2 is connected between lines C and B. Find the following:

The phase current $\overline{I_{AB}}$ at the load =

$4\angle 0^\circ \text{ A}$

The Line current $\overline{I_A}$ =

$6.08\angle 25.3^\circ \text{ A}$

The Line current $\overline{I_C}$ =

$7.94\angle 79.1^\circ \text{ A}$

The reading of W_1 =

1.32 KW

The reading of W_2 =

1.8 KW

The total power dissipated in the load =

3.12 KW

Question #5: (14 Points)

The voltage source v_g drives the circuit shown in Fig.5. The response signal is the voltage across the capacitor, v_o .

- a) Calculate the numerical expression for the voltage transfer function $H_v(s) = V_o(s)/V_g(s)$. (6 points)
- b) Calculate the numerical values for the poles and zeros of the transfer function. (4 points)
- c) The circuit is driven by a step voltage source, namely, $v_g = 50u(t)$, find $v_o(t)$. (4 points)

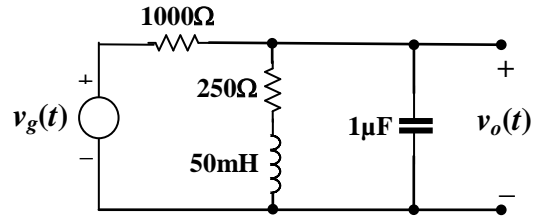


Fig.5

$$H_v(s) = \frac{1000(s + 5000)}{s^2 + 6000s + 25 \times 10^6}$$

Poles: $-3000 + j4000, -3000 - j4000$

Zeros: $-5000, \infty$

$$V_{out}(t) = [10 + 11.18 e^{-3000t} \cos(4000t - 153.4^\circ)]u(t) \text{ V}$$

Question #6: (12 Points)

The ideal transformer used in the circuit of Fig.6 has a turns ratio $N_2/N_1 = 3$.

- a) Find the reflected impedance at terminals a-b of that transformer. (6 Points)
- b) Calculate the value of the currents I_1, I_2, I_3 , and I_4 . (6 Points)

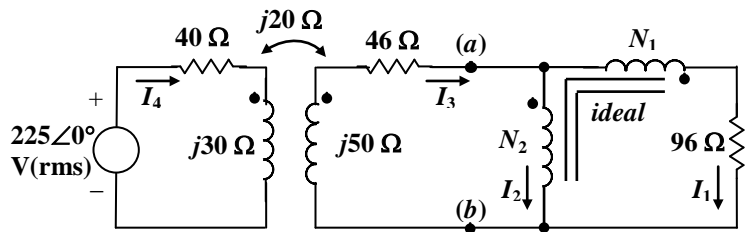


Fig.6

$$Z_R = \left(\frac{a}{1+a}\right)^2 R_L = 54\Omega$$

$$I_1 = 0.584 \angle 30.1^\circ \text{ A}$$

$$I_2 = 0.195 \angle 30.1^\circ \text{ A}$$

$$I_3 = 0.779 \angle 30.1^\circ \text{ A}$$

$$I_4 = 4.35 \angle -33.3^\circ \text{ A}$$

Question #7: (6 Points)

- a) Calculate the impedance of the circuit shown in Fig.7 at radian frequency of 2 Krad/S. (2 Points)
- b) At what finite frequency (ω_r) does the impedance of the circuit become purely resistive? What is the impedance at that frequency? (4 Points)

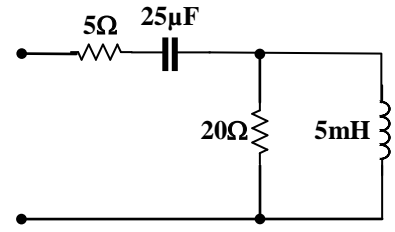


Fig.7


$Z(2\text{Krad}) = 9 - j12 \Omega$

$\omega_r = 4 \text{ Krad/S}$

$Z(\omega_r) = 15 \Omega$

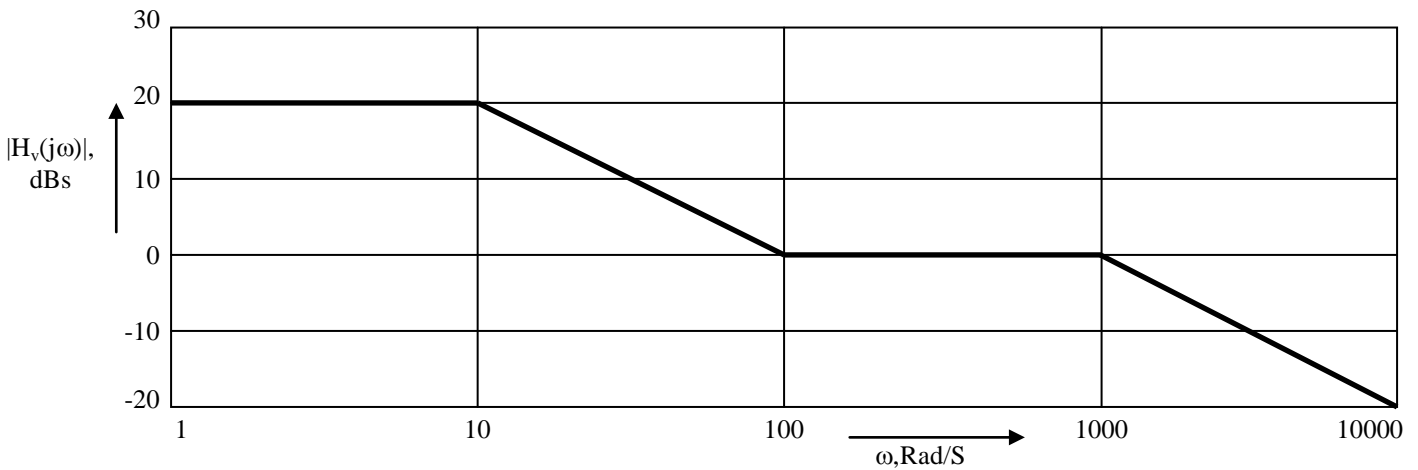Question #8: (8 Points)

Sketch the Bode Diagram of the voltage transfer function: $H_v(s) = \frac{1000(s + 100)}{(s + 10)(s + 1000)}$



Question #9: (8 Points)

The y parameters for the two-port network in Fig.9 are: $y_{11} = 2\text{mS}$, $y_{12} = -0.2\text{mS}$, $y_{21} = 10\text{mS}$, and $y_{22} = -0.5\text{mS}$. Find V_1 , V_2 , I_1 , and I_2 .

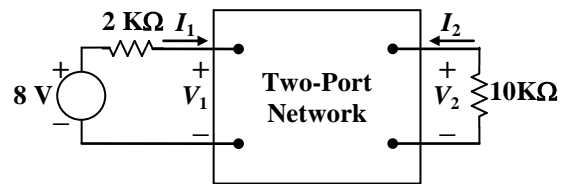


Fig.9

$V_1 = -1.6 \text{ V}$

$V_2 = -40 \text{ V}$

$I_1 = 4.8 \text{ mA}$

$I_2 = 4 \text{ mA}$