

Electric and Electronic Circuits (جميع الطلاب)

Answer all questions: (Total Marks 100)

Q1: The circuit shown in Fig.1 has three components with indicated loads.

- Calculate the total complex power (S) absorbed (4 Marks)
- Calculate the supply current. Will the circuit breaker trip or not and why? (3 Marks)
- What is the total impedance of the network? (3 Marks)

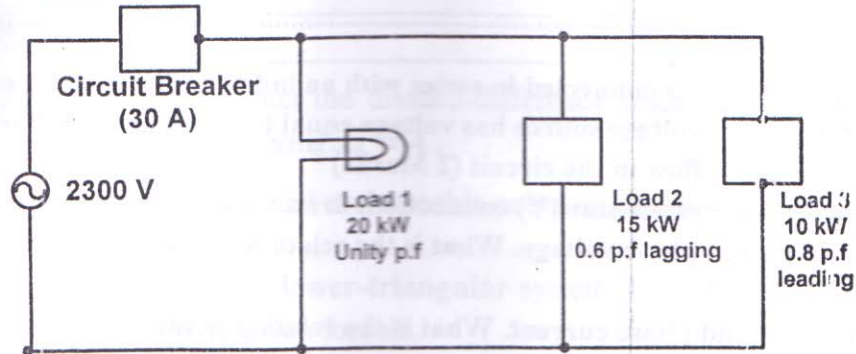


Fig.1

Q2: For the circuit shown in Fig.2, Find:

- I using loop analysis method (10 Marks)
- Check your answer using node analysis method (8 Marks)
- Check power balance in the circuit. (7 Marks)

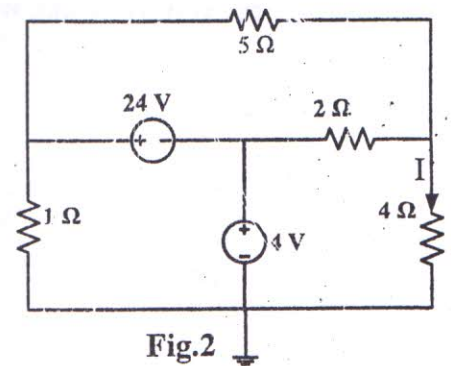


Fig.2

Q3: For the circuit shown in Fig.3, Find:

- Norton equivalent (I_N and R_N) (10 Marks)
- The resistance R_L to be connected between a and b to absorb maximum power (5 Marks).
- Calculate the maximum power (5 Marks)

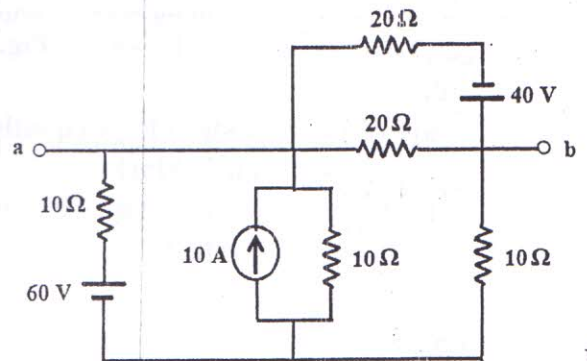


Fig. 3

انظر خلف

Q4: For the circuit shown in Fig.4, find:

- Current I_T (5 Marks)
- I_1, I_2, I_3 (9 Marks)
- Check active power balance in the circuit (3 Marks)
- Check reactive power balance in the circuit (3 Marks)

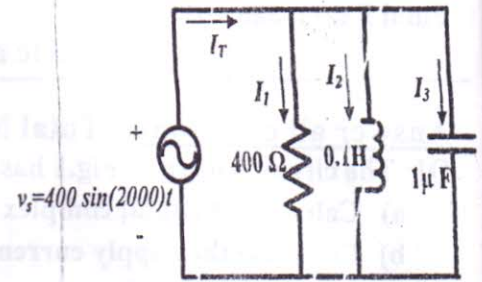


Fig. 4

Q5:

- If a 30Ω resistance is connected in series with an inductor 1 mH and a capacitor $1 \mu\text{F}$ and supplied from DC voltage source has voltage equal to 220 V , what will be the maximum and minimum current flow in the circuit (2 Marks)
- In a three- phase system star (Y) connection, draw the connection and indicate the following
 - Line voltage and phase voltage. What is the relation between line and phase voltages (2 Marks)
 - Line current and phase current. What is the relation between line and phase currents (2 Marks)
- Find the time period (T), frequency, average value and root mean square (effective) values of the voltage signal, which it is shown in Fig.5 (4 Marks)

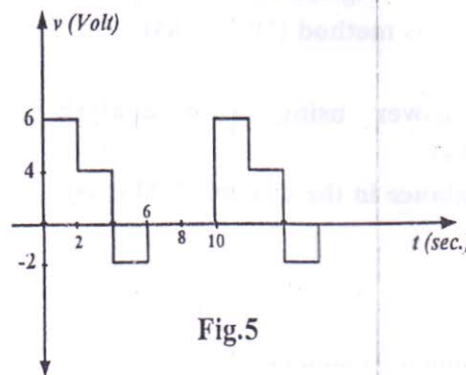


Fig.5

Q6: For the circuit shown in Fig. 6, find:

- Write the node voltage equations of the circuit (5 Marks)
- Find voltage V_{ab} using Thevenin Theory (10 Marks)

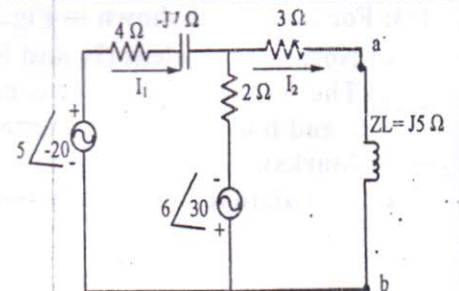


Fig.6

Good Luck

Dr. Aboelsood A. Zidan & Dr. Hassan Mohamed, Jan.2015