

✓ تاريخ



Fig. Q4



Fig. Q5-a

$V_G = 25 \text{ V}$, R_G
same V_{in} is va

Answer All Questions. The solution must include the necessary equations, curves and connections diagrams. **(Max. Marks : 50)**

1) Give an account about :

- # Failure of excitation and re-excitation in self- excited dc generators.
- # Comparison between the short-shunt dc generator and long-shunt differential dc motor.
- # The unstable ranges in the external characteristic of dc generators .
- # Two methods used for speed control of each shunt and series dc motors . **(11 Marks)**

2) A short-shunt dc motor , $2p=8$, 240 V , 70 A , 19 BHP has 200 conductors in the armature . The armature slot contains 4 coil sides , each coil side has 2 conductors . The no load air-gap flux = 0.03 Wb .

$R_{fs} = 0.2 \Omega$, $R_a = 0.1 \Omega$, $R_f/\text{pole} = 10 \Omega$ and $R_g = 33 \Omega$.

At rated load , the air-gap flux becomes 95 % of its value at no load due to the AR effect.

- # Find S , C , number of commutator segments and brushes , the type of winding used and its pitches ?
- # Draw a sketch of the developed diagram of the used winding ?
- # At rated values ; calculate the speed of the motor , the developed torque in kg.m (state its name ?) , P_{ML} and efficiency ? (Neglect saturation) . **(12 Marks)**

3) The OCC of a separately-excited dc generator at 800 rpm is

I_f / A	0.4	0.6	0.8	1.0	1.2	1.4	1.6	1.8	2.0
E / V	150	220	250	265	275	282	290	295	300

If the generator feeds a load at 1000 rpm , obtain its OCC and draw it only ?
The generator is excited from 225 V mains and has $R_a = 0.2 \Omega$, $R_{fc} = 125 \Omega$.
At the speed 1000 rpm and $I_a = 100 \text{ A}$, the AR reduces the induced emf by 22 V .
Find the load voltage , load resistance and draw the load line .
At 1000 rpm and the load current = 70 A , calculate the load voltage regulation and the developed torque in kg. m. (state its name) . **(9 Marks)**

P T O

[Signature]



✓

4) A 100 V , 1500 rpm shunt dc generator has OCC as

I_f / A	0	0.5	1.0	1.5	2.0	2.5	3.0	3.5	4.0	4.5	5.0	5.5
E / V	3	22.5	45	67.5	88	100	108	113	116	118	120	122

The O C voltage = 120 V and $R_a = 0.2 \Omega$.

At full-load , the voltage drop due AR equals 5 V .

Calculate R_{fc} and the short circuit current ?

Find I_a at full-load and the load resistance ?

Find the voltage regulation at half full-load armature current ?

Calculate the critical resistance of the shunt field circuit at 1500 rpm and also the critical speed ?

(9 Marks)

5) A 9 HP , 220 V , 35 A , 300 rpm dc series motor has $R_a = 0.1 \Omega$ and $R_{fs} = 0.05 \Omega$.

Find at full-load the P_{ML} and output torque in N.m.

At constant supply voltage , a diverter resistance of 0.08Ω is used . The developed torque becomes 0.75 of its full-load value . Calculate the new value of the armature current and speed, then find the efficiency. Take $P_{ML} \propto N$.

(Neglect AR and saturation)

(9 marks)

Prof. Hassan I. Abou-faddan

End of Questions